


Lecture 22

Friday, 12 April 2024 3:33 PM

EE114 - Power Engineering 1

Course instructor: Prof. Sandeep Anand


Scribe: Saurabh Singh

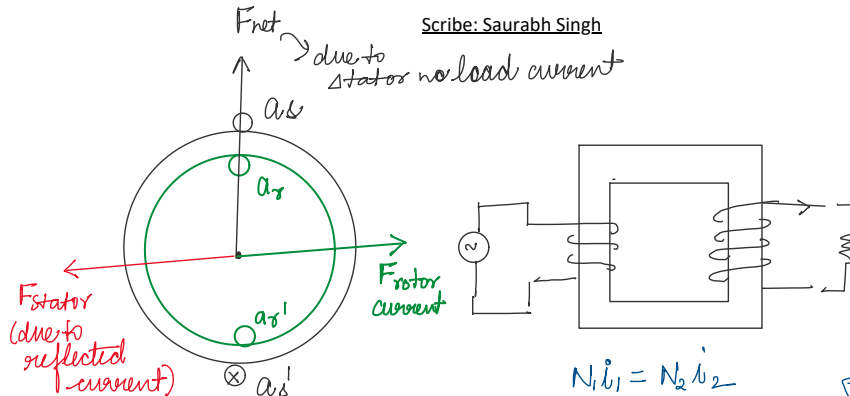


Consider the snapshot of the induction motor. The net MMF (F_{net}) is vertical. The F being linked to coil is 0, the voltage induced is maximum in rotor winding. It produces a large current producing a rotor flux in horizontal direction (F_{rotor}). To keep the net flux unchanged, stator produces a reflected current. (Draw the analogy from transformer)

$$N_s I_s = I_s' N_s$$

Stator side:-

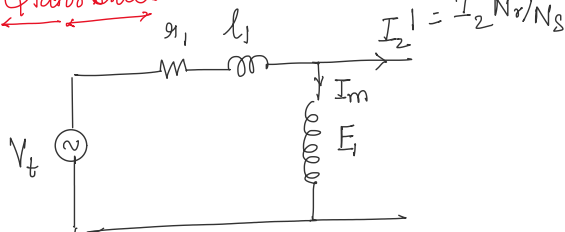

Rotor side

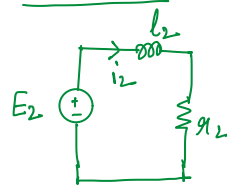

$$E_1 = 4.44 N_f \phi_m$$

$$E_2 = 4.44 N_2 \Delta f_1 \phi_m$$

$$= 8 (4.44 N_2 f_1 \phi_m) = I_2 \times \sqrt{r_2^2 + (s l_2 \omega_1)^2}$$

$$E_1 = \frac{E_2 N_1}{8 N_2}$$

Stator

$$\frac{E_1}{N_1} = \frac{E_2}{s N_2}$$

Rotor


$$E_1 = \frac{N_1}{8 N_2} I_2 \sqrt{r_2^2 + (s l_2 \omega_1)^2}$$

$$= \frac{N_1}{8 N_2} \times \frac{N_1}{N_2} I_2' \sqrt{r_2^2 + (s l_2 \omega_1)^2}$$

$$E_1 = I_2' \sqrt{\left(\frac{r_2'}{s}\right)^2 + (\omega l_2')^2}$$


$$r_2' = r_2 \left(\frac{N_1}{N_2}\right)^2$$

Equivalent ckt:-

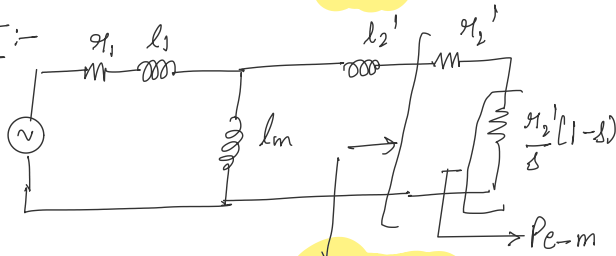

$P_{ag} \rightarrow P_{airgap}$
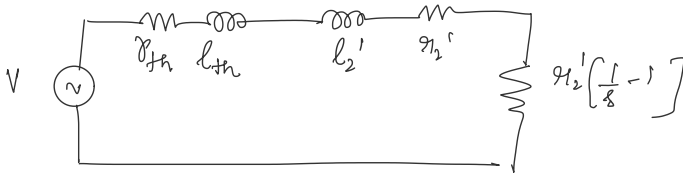
$$P_{e-m} = 3 I_2'^2 \frac{r_2' (1-s)}{s}$$



$$\omega_r T_{em} = 3 I_2'^2 \frac{r_2' (1-s)}{s}$$

$$s = \frac{\omega_1 - \omega_r}{\omega_1}$$


$$\omega_r = (1-s)\omega_1$$

$$\tilde{I}_{em} (1-s) \omega_1 = 3 I_2'^2 \frac{r_2' (1-s)}{s}$$

$$T_{em} = \frac{3}{\omega_s} \left[\frac{V_{th}^2}{\left(r_{th} + \frac{r_2'}{s} \right)^2 + (X_{th} + X_2')^2} \right] \times \frac{r_2'}{s}$$

When $s \rightarrow 0$
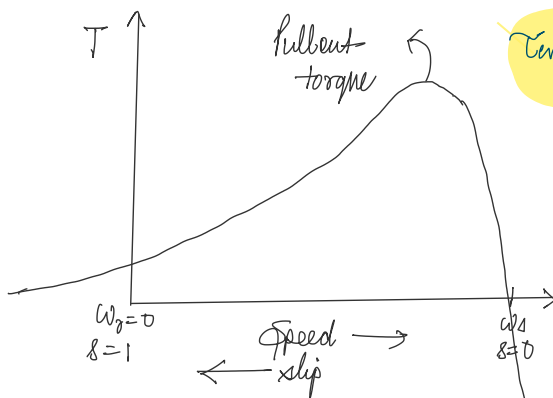
$$T_{em} = \frac{3}{\omega_s} \frac{V_{th}^2}{r_{th}^2} \times s$$



At starting the induction motor draws large current because at starting $s=1$.