

## Lecture 19

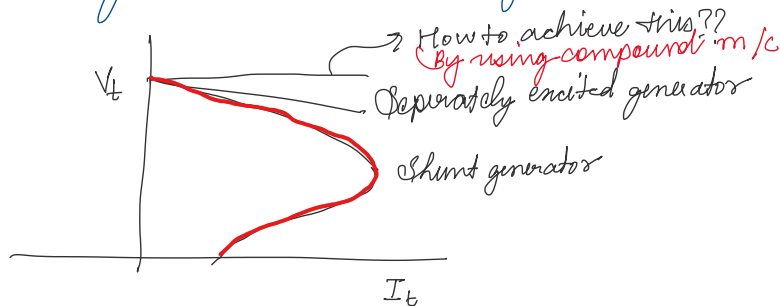
Tuesday, 26 March 2024 3:34 PM

EE114 - Power Engineering 1Course instructor: Prof. Sandeep AnandScribe: Saurabh Singh


\* Separately excited DC machine

$\rightarrow I_f$   
 $\rightarrow \text{Armature} \rightarrow \text{O/C}$   
 $I_a = 0$

Copper losses are combined in Rotational loss or mechanical loss

\* Lap winding -  $a = p$  ; Wave winding -  $a = 2$ 

\* DC Motor :-

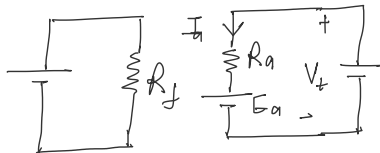

Separately excited DC motor

Shunt DC motor has nearly the same characteristics. So we will only focus on separately excited motor.


$$V_t - I_a R_a = E_a$$

$$T_e = k \phi I_a$$

$$E_a = k \phi \omega$$

$$V_t - \frac{T_e}{k \phi} R_a = k \phi \omega$$

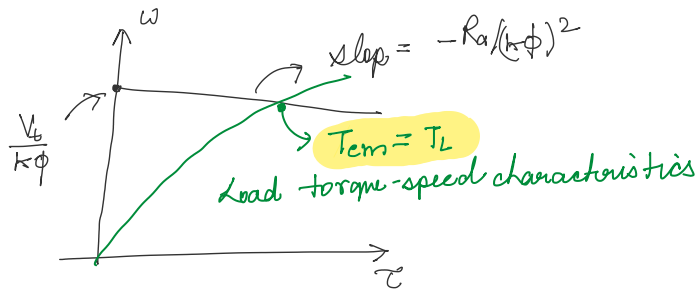
$$\omega = \frac{V_t}{k \phi} - \frac{R_a}{(k \phi)^2} T_e$$



Load characteristics of fan, water pump  $T \propto \omega^2$   
 Friction  $T \approx \text{const}$


Now suppose we change the speed of motor

Method ①

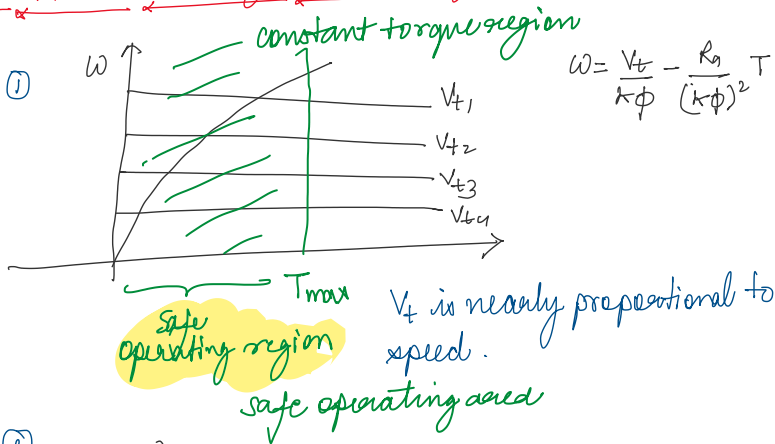

Method ②

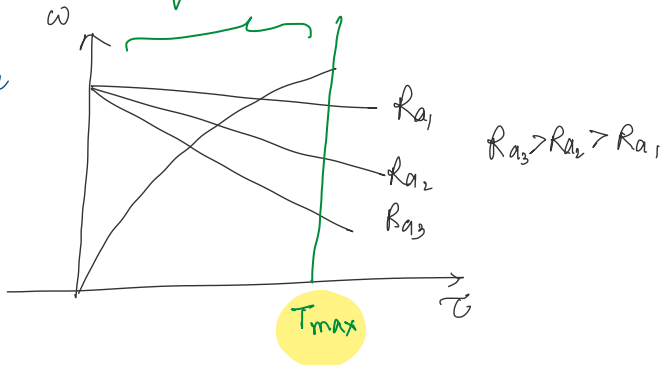Inject Resistance  
in armature  
winding



$T_{max} = ?$

Method ③

Have a variable  
flux

Flux or field  
weakening

Constant power  
region




Safe operating region is limited by max power.

At base speed  $\rightarrow V_t \rightarrow \text{nominal}, \phi \rightarrow \text{rated}, \text{Rated Load}$

At start  $\rightarrow \phi \rightarrow \phi_{rated}$   
 $V_t \rightarrow$  very small

At base speed  $\rightarrow \phi \rightarrow \phi_{rated}$   
 $V_t \rightarrow V_{t rated}$

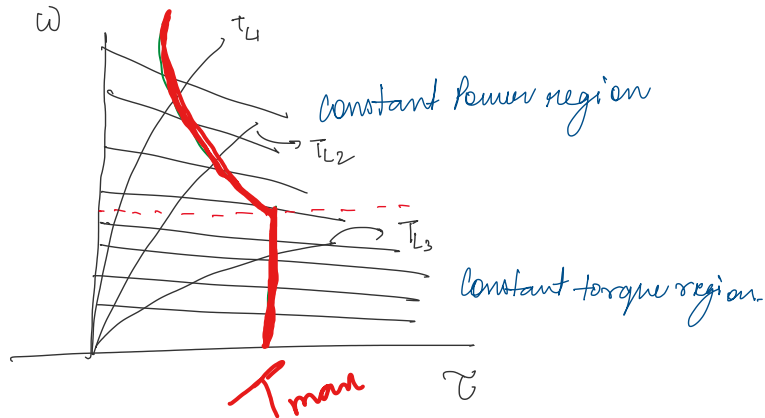At above base speed  $\rightarrow \phi < \phi_{rated}$   
 $V_t \rightarrow V_{t rated}$



$\omega \tau = \text{power}$