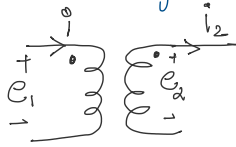


Lecture 11


Wednesday, 14 February 2024 9:42 AM

EE114 - Power Engineering 1Course instructor: Prof. Sandeep AnandScribe: Saurabh Singh


Consider an ideal transformer :-

We now know $\frac{E_2}{E_1} = \frac{N_2}{N_1}$ & $I_2 N_2 = I_1 N_1$

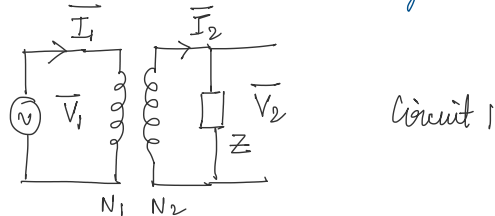Now let's connect a load to secondary side



Consider another circuit

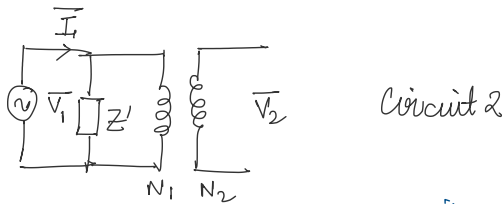

Circuit 1 & circuit 2 are equivalent if

 I_1 in both circuits are same \Rightarrow same source current& V_2 in both circuits are same

Same i/p & o/p characteristics



& Z is said to be referred to the primary side $\Rightarrow Z' \rightarrow Z$ referred to primary sideIn circuit 1 $\rightarrow I_2 = \frac{V_2}{Z}$ & $I_1 = \frac{V_2}{Z} \frac{N_2}{N_1}$ & $I_1 = \frac{N_2^2}{N_1^2} \frac{V_1}{Z}$ In circuit 2 $\rightarrow I_1 = \frac{V_1}{Z'}$

If in both circuits source current is same

$$\frac{V_1}{Z'} = \frac{N_2^2}{N_1^2} \frac{V_1}{Z}$$

$$Z' = \left(\frac{N_1}{N_2} \right)^2 Z$$

Now consider another circuit

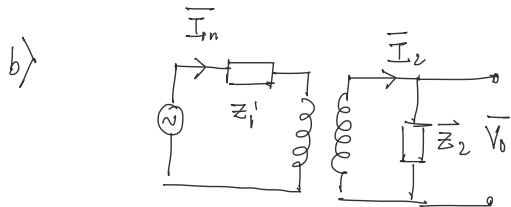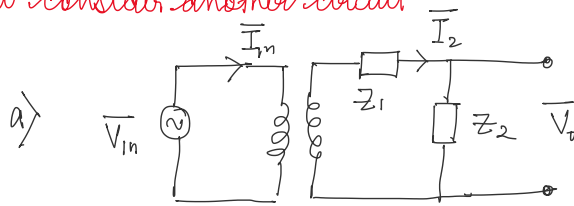

In figure (a)

$$V_o = V_{in} \times \frac{N_2}{N_1} - I_2 Z_1$$

$$V_o = V_{in} \frac{N_2}{N_1} - I_2 Z_1 \quad \text{--- (i)}$$

$$V_o = I_2 Z_2$$

both have same secondary current

If figure (b)


$$V_o = I_2 Z_2$$

$$V_o \frac{N_1}{N_2} = V_{in} - I_{in} Z_1'$$


$$\Rightarrow V_o = V_{in} \frac{N_2}{N_1} - \frac{N_2^2}{N_1^2} Z_1' I_2 \quad \text{--- (ii)}$$

From (i) & (ii)

$$Z_1' = \frac{N_1^2}{N_2^2} Z_1$$

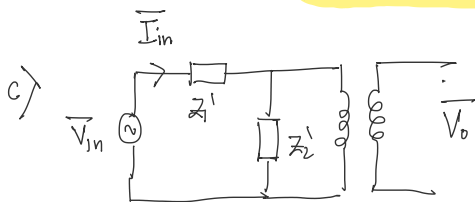

* Actual transformer :-

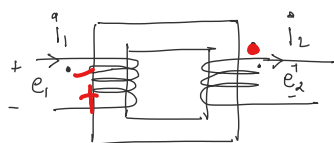

* Let μ is not infinite

$$e_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$\int e_1 dt = L_1 i_1 - M i_2$$


$$M = \frac{N_1 N_2}{R}$$

$$L_1 = \frac{N_1^2}{R}$$

$$i_1 = \frac{1}{L_1} \int e_1 dt + \frac{M}{L_1} i_2$$

$$\frac{M}{L_1} = \frac{N_2 N_1}{N_1^2}$$
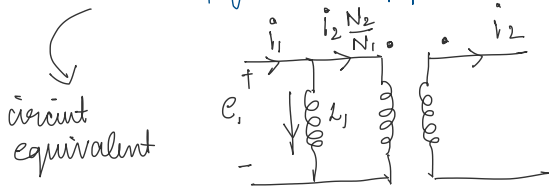
$$i_1 = \frac{1}{L_1} \int e_1 dt + \frac{N_2}{N_1} i_2$$



Circuit equivalent of transformer with finite μ .

L_1 branch \rightarrow magnetizing inductance


The current in magnetizing inductance is magnetizing current.

If μ is considered to be infinite $L_1 \rightarrow$ infinite then magnetizing current is zero. It's as if magnetizing branch is not at all there. We go back to ideal transformer.

$$L_m = L_1 = \frac{N_1^2}{R_1}$$


Primary current has 2 components, magnetizing current & secondary side current referred to primary side.

Leakage

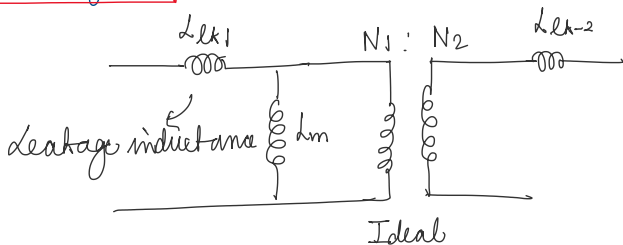

Losses

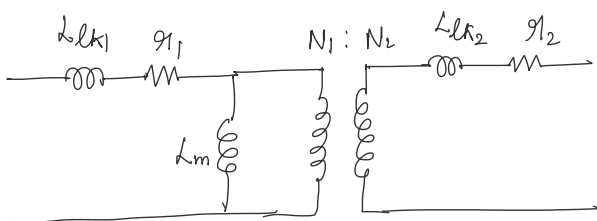
(i) losses in winding \rightarrow Copper loss or conduction losses




(ii) eddy current:— the flux the produces voltage in coil, also induces voltage in core. It leads to circulating current. The energy gets dissipated as heat.

We want to get rid of eddy current losses
→ we use laminated cores.

(iii) Phytocorisides:-

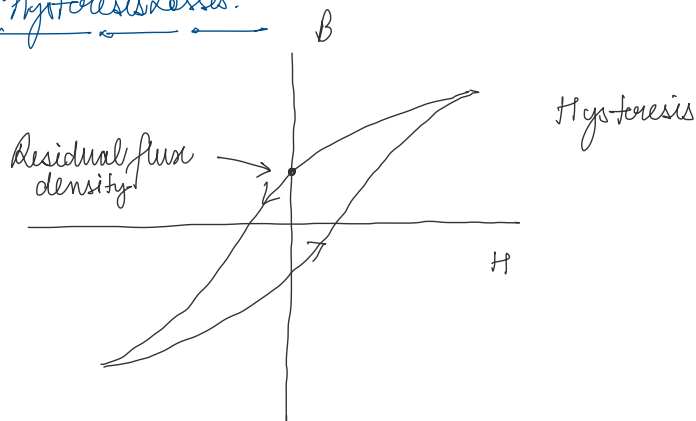

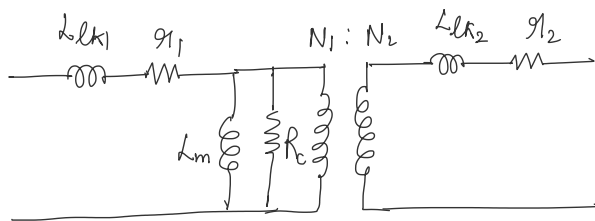We take one path going up the B-H curve & another path while coming down. Energy is consumed in this process.



Core losses \rightarrow eddy current loss
 \rightarrow hysteresis loss

$$\text{Eddy loss} = K_e B_m^2 f^2 t^2 V$$

$$\text{Hysteresis loss} = \eta B_m^h f v$$

It is represented as shunt because this is dependent on voltage induced in core. voltage induced is dependant on flux. which further depends upon applied voltage.

~~eddy current loss $\propto V^2 f$~~
~~hysteresis loss $\propto V f (\oint B H) \rightarrow \text{Area of BH loop}$~~
~~Volume $\propto V f B_m^n$~~

$n \rightarrow 1 \text{ to } 2$
 typical 1.5
 1.6