
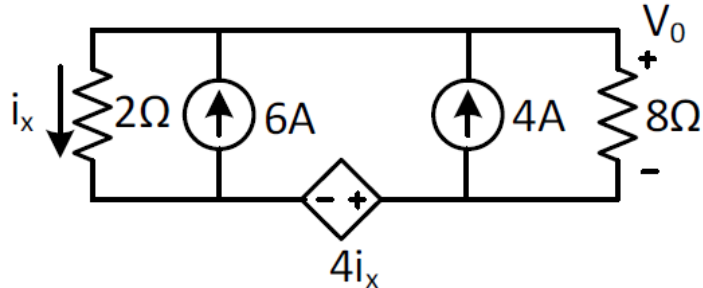

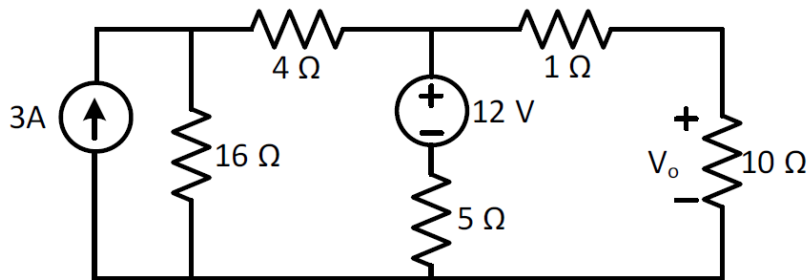
## Assignment 1


- ★ 1. Consider the following circuit. Find voltage using Thevenin theorem. Cross verify your answer by Superposition Theorem. (Ans=-26.67V)



2. Find  $V_o$  of the following circuit by applying Mesh Analysis. Cross verify your answer by applying Thevenin Theorem. (Ans:  $V_o=12.8V$ )



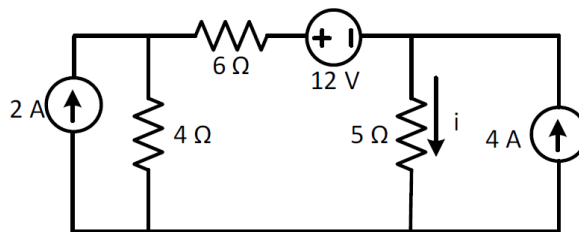3. Find the current  $i$  of the following circuit. (ans:  $i=2.4A$ )



4. Write the following AC signals in phasor form:-

a)  $v(t) = 311 \sin(314t - 0.139\pi) V$

Convert into  $\cos(\theta)$  and then find the angle.

b)  $i(t) = 10 \sin\left(10t + \frac{\pi}{3}\right) + 15 \sin\left(10t - \frac{\pi}{6}\right) A$

c)  $i(t) = 460 \sin(500\pi t - 0.139\pi) - 220 \cos\left(500\pi t + \frac{\pi}{12}\right) A$

(Ans. (a)  $\bar{V} = 219.9 \angle -115^\circ$ , (b)  $\bar{I} = 12.746 \angle -86.31^\circ$ , (c)  $\bar{I} = 441.64 \angle -130.65^\circ$ )

5. Find the time domain expression corresponding to each of the following phasor.  
 $(\omega = 314 \text{ rad/sec})$

a)  $\bar{I} = (10 \angle 30^\circ + 25 \angle 60^\circ) \text{ mA}$

b)  $\bar{V} = (60 + j30 + 100 \angle -28^\circ) \text{ V}$

(Ans (a)  $i(t) = 48.12 \cos(314t + 0.286\pi) \text{ mA}$ , (b)  $v(t) = 211.1 \cos(314t - 0.036\pi) \text{ V}$ )

6. A series RLC circuit is composed of  $10 \Omega$  resistor, a  $0.1 \text{ H}$  inductor and a  $50.0 \mu\text{F}$  capacitor. A voltage  $v(t) = 141.4 \cos(377t) \text{ V}$  is applied across the RLC circuit.

a) Find the phasor current in the circuit.

b) Find the expression for the instantaneous current.

c) Calculate the voltage drops  $V_R$ ,  $V_L$  and  $V_C$  across the resistor, inductor and capacitor respectively.

Ans: (a)  $I = 5.45 \angle 56.9^\circ \text{ A}$


(b)  $i(t) = 7.7 \cos(377t + 0.316\pi) \text{ A}$

(c)  $V_R = 54.5 \angle 56.9^\circ \text{ Volts}$ ,  $V_L = 205.46 \angle 146.9^\circ \text{ Volts}$ ,  $V_C = 289.12 \angle -33.1^\circ \text{ Volts}$

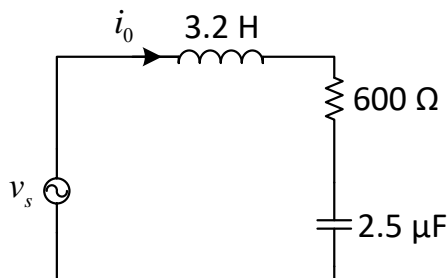7. Find the value of  $\omega$  for the circuit given, is operating in steady state and


$$v_s = 40 \sin\left(\omega t + \frac{\pi}{12}\right) \text{ V}$$

$$i_0 = 40 \cos(\omega t - 0.712\pi) \text{ mA}$$



(Ans.  $\omega = 500 \text{ rads}^{-1}$ )

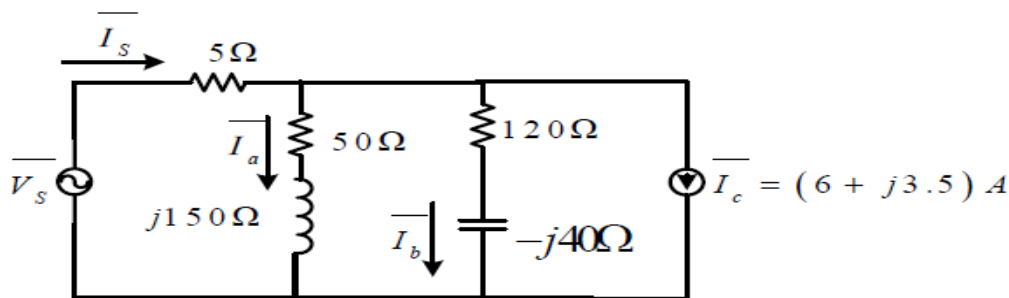
8. The current  $\bar{I}_b$  in the circuit, shown is Fig., is  $5 \angle 0^\circ \text{ A}$ .




(a) Find  $\bar{I}_a$ ,  $\bar{I}_s$  and  $\bar{V}_s$ .

Ans.  $\bar{I}_a = 4 \angle -90^\circ \text{ A}$ ,  $\bar{I}_s = 11.01 \angle -2.6^\circ \text{ A}$ ,  $\bar{V}_s = 685.58 \angle -17.18^\circ \text{ V}$

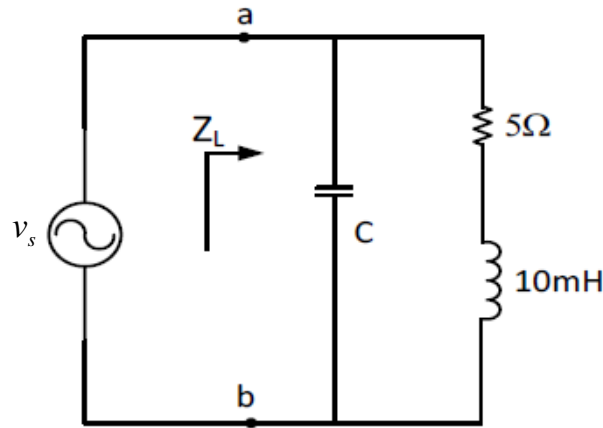9. A source ( $\omega = 314 \text{ rad/s}$ ) is connected to a load  $Z_L$  as shown in below Fig. Find the value of the capacitance for the load  $Z_L$  to be completely resistive. What is the actual impedance that the source see with this value of the capacitor?  
(Ans.  $C = 287 \mu\text{F}$ ,  $Z = 6.97 \Omega$ )



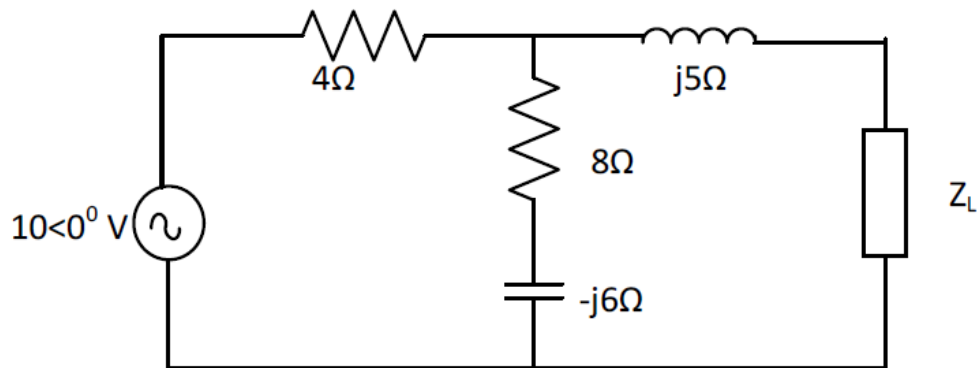
10. Determine the maximum value of  $Z_L$  that maximizes the average power drawn from the ckt of below Fig. What is the maximum power? (Ans: 4.74 W).



11. A single phase load draws apparent power of 250 kVA at power factor 0.80 lagging,  
(a) How many kVAr of capacitors must be added to improve this power factor to 0.90 lagging?  
(b) After improvement of the power factor, a new load is to be added at 0.50 lagging power factor. How many kVA of this new load will bring the total cumulated load back to 250 kVA, and what will be the final power factor?  
(Ans: (a) 53.14 kVAr, (b) kVA of new load = 32.75 and PF = 0.8655)

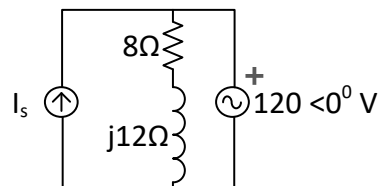12. Determine the current  $I_s$  in the circuit. Provided the voltage source supplies 2.5 kW  
(Ans:  $19.19 \angle -147.69^\circ \text{ A}$ )


Capacitor and Inductive power get subtracted. Capacitor generates imaginary power while inductor dissipates it.



Calculate the angle with x-axis only and if calculated along some other axis, then convert it with respect to x-axis.

13. Determine the complex power delivered to  $10\ \Omega$  resistance.


(Ans:  $S=51\angle 2\text{ mVA}$ )

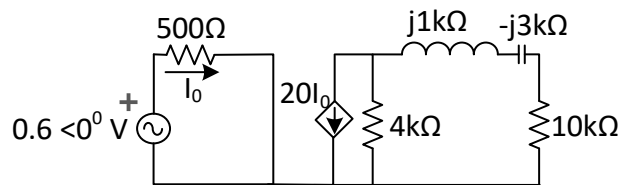

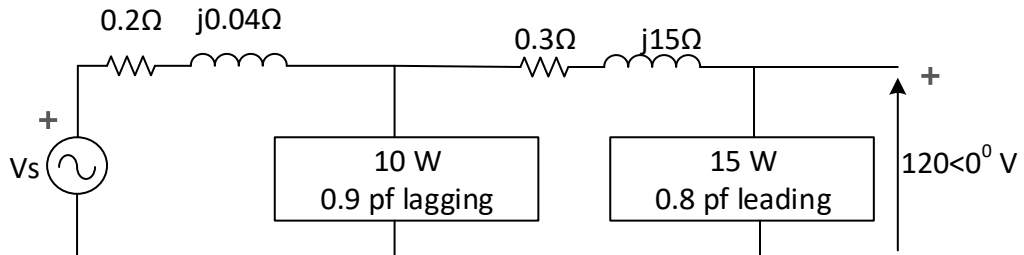14. Find  $V_s$


(Ans:  $V_s=120.06\angle 0.03^\circ\text{ V}$ )

While assigning the sign for the imaginary part, always check whether the element is leading or lagging.



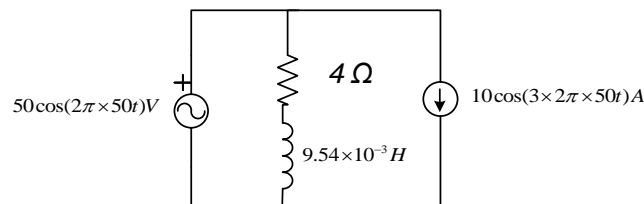15. Find the average real and reactive power delivered by the voltage source for the given circuit. Also find the power factor of the voltage source

(Ans:  $P=200\text{W}$ ,  $Q=291.54\text{ VAR}$ ,  $\text{pf}=0.565$ )



16. Three loads are connected in parallel to a  $120\angle 0^\circ\text{ V}$  source. Load 1 absorbs  $60\text{ kVAR}$  at  $0.85\text{ pf}$  lagging, Load 2 absorbs  $90\text{ kW}$  and  $50\text{ kVAR}$  leading and Load 3 absorbs  $100\text{ kW}$  at  $1\text{ pf}$ . Find the equivalent impedance of the circuit and current supplied by source. (ans:  $Z=0.05014+j0.00175\text{ ohms}$ , and  $I_s=2.392\angle -2^\circ\text{ kA}$ ).

17. Two loads are connected in parallel to a  $120\angle 0^\circ\text{ V}$  source. Load 1 absorbs  $24\text{ kW}$  at  $0.8\text{ pf}$  lagging, Load 2 absorbs  $90\text{ kW}$  at  $0.95\text{ pf}$  lagging. Find the value of the capacitance connected in parallel that'll improve the pf of the system to unity. (ans:  $C=10.51\text{ mF}$ ).