



Lecture 14

Tuesday, 5 March 2024 3:35 PM

EE114 - Power Engineering 1

Course instructor: Prof. Sandeep Anand

Scribe: Saurabh Singh

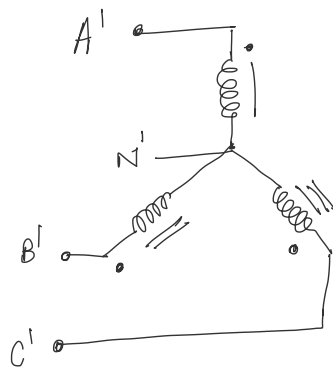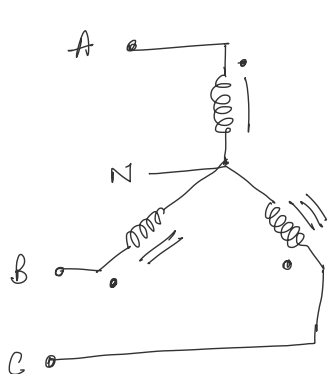* 3-phase transformers :-1. Y-Y connection

Here the voltage difference across the coupled coils is same.

(i)



$$\angle \frac{V_{AB}}{V_{A'B'}} = 0$$

(No phase shift b/w \bar{V}_{AB} & $\bar{V}_{A'B'}$)

$$n = \frac{N_2}{N_1} \text{ (effective turns ratio)}$$

(ii)

$$V_{A'N'} = \frac{N_2}{N_1} V_{AN}$$

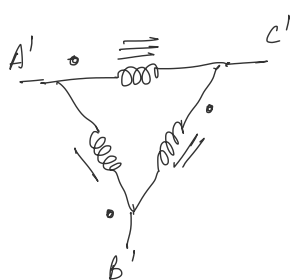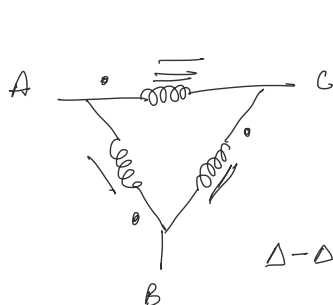
2. Δ - Δ connection :-

effective turns ratio

$$n = \frac{V_{A'B'}}{V_{AB}} = \frac{N_2}{N_1}$$

No phase shift
b/w \bar{V}_{AB} & $\bar{V}_{A'B'}$

Y-Δ connection

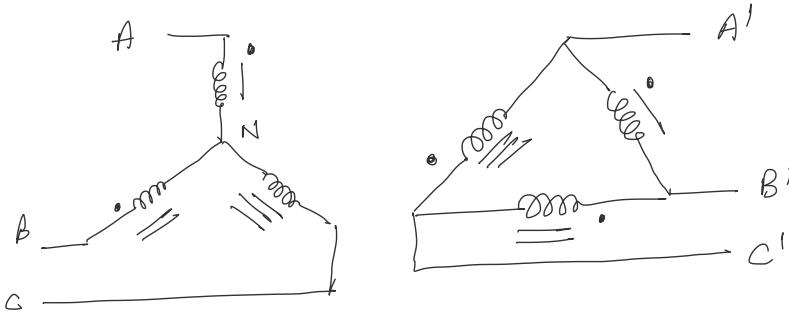

$$\overline{V_{A'B'}} = \frac{N_2}{N_1} \overline{V_{AN}}$$

$$\overline{V_{AB}} = \frac{N_2}{N_1} \frac{1}{\sqrt{3}} \overline{V_{AB}} \angle -30^\circ$$

$$\eta = \frac{\overline{V_{A'B'}}}{\overline{V_{AB}}} = \frac{N_2}{N_1} \frac{1}{\sqrt{3}} \angle -30^\circ$$

Popular configuration




We need neutral on distribution side.

* Open Delta :-


Improves availability of supply

* Practical 3 φ transformers :-

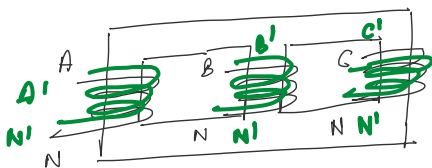

* Distribution system :-

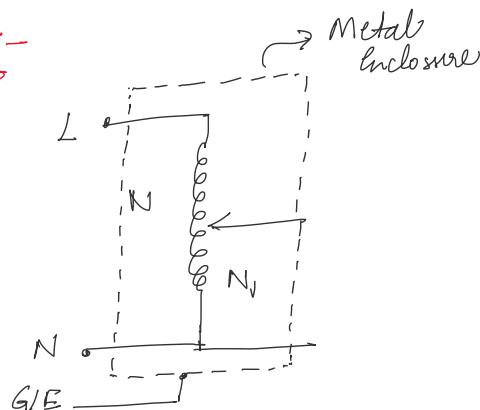
Any metal enclosure has to be earthed (physically earthed) to avoid shock due to static charge.



Also if line wire is damaged & touches the metal enclosure and the enclosure is not earthed then if someone touches it, the person may

receive a serious shock.

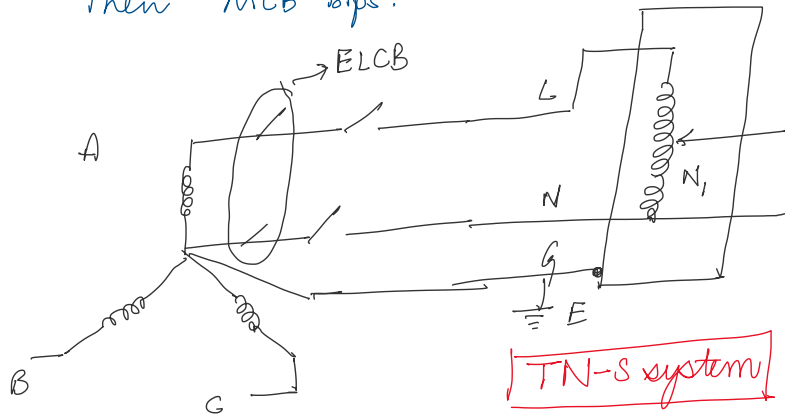If earthed then large current flows for L to E
Then MCB trips.



If someone accidentally touches live wire, a net current flows through LN, which is detected by ELCB (earth leakage ckt. breaker) and breaks the circuit.

