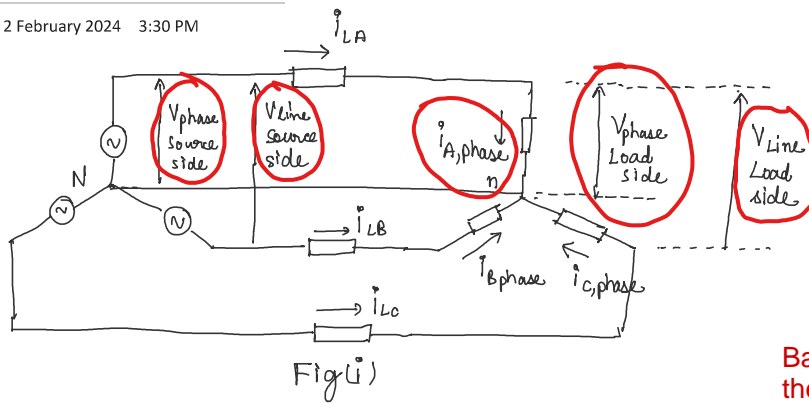


Lecture 7

Friday, 2 February 2024 3:30 PM



Phase voltage and current can be defined for load side and source side.


In the above figure with star connected load

(i) Line current = Load side phase current
 $\checkmark \quad \bar{I}_{A,phase} = \bar{I}_{LA}$

(ii) And at load side

$$\sqrt{3} \bar{V}_{phase, An} \angle 30^\circ = \bar{V}_{AB} \quad \checkmark$$


for delta connected loads :-

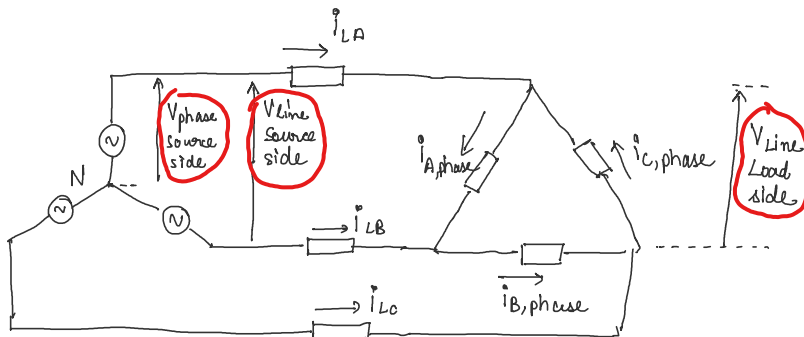

(i) $\bar{V}_{line (load side)} = \bar{V}_{phase (load side)}$

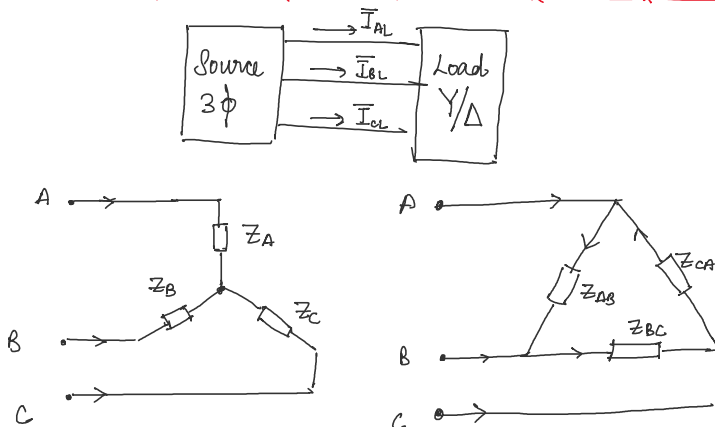(ii) $\bar{I}_{LA} = \bar{I}_{A,phase} - \bar{I}_{C,phase}$

* Conversion from star load to delta load & vice-versa :-



Balanced means that everything is same but the theta values are different.

Most of our formulas are for ideal or particular cases and so learn the concepts and not the formulas.

When doing these questions, first make a rough diagram and deduce all the circuit related properties and then start solving the question. Write the required variables in terms of the known ones. Take time but do correctly.

Impedance b/w AB in $\dot{Y} = Z_A + Z_B$

Impedance b/w AB in $\Delta = \frac{Z_{AB}(Z_{BC} + Z_{CA})}{Z_{AB} + Z_{CA} + Z_{BC}}$

$$\Rightarrow Z_A + Z_B = \frac{Z_{AB}(Z_{BC} + Z_{CA})}{Z_{AB} + Z_{CA} + Z_{BC}} \quad \text{--- (i)}$$

Similarly $Z_B + Z_C = \frac{Z_{BC}(Z_{AB} + Z_{CA})}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (ii)}$

6 $Z_C + Z_A = \frac{Z_{CA}(Z_{AB} + Z_{BC})}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (iii)}$

Using the above three equations :-

$$Z_A = \frac{Z_{AB} Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_{AB} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_C}$$

Source can be star or delta too.

* Total complex power $S_{3\phi} = S_A + S_B + S_C$
($P + jQ$)

In case of a balanced system $S_A = S_B = S_C$

$$S_{3\phi} = 3 S_A$$

$$S_{A-source} = \overline{V_{AN}} \overline{I_A}^*$$

$$P_{A-source} = |\overline{V_{AN}}| \times |\overline{I_A}| \cos \theta$$


where θ is the angle b/w phase voltage & line current

$$P_{3\phi} = 3 V_{ph} I_L \cos \theta$$

$$P_{3\phi} = \sqrt{3} V_L I_L \cos \theta$$


Why not only delta?

* Wattmeter :-

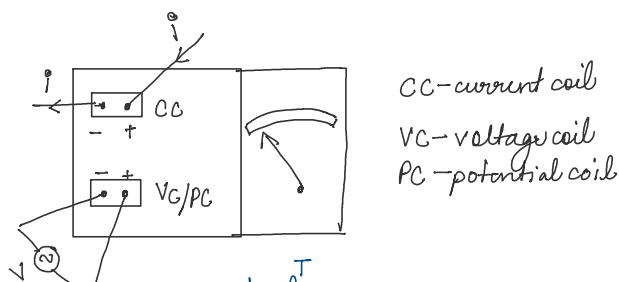


$$W = \frac{1}{T} \int_0^T v i dt$$

$$= V_{rms} I_{rms} \cos \theta$$

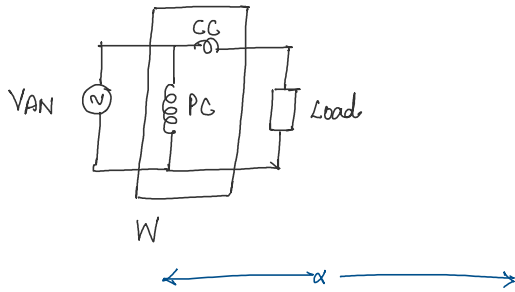

* How do you measure in a 3-phase circuit??


Case 1:- 4 wire balanced system

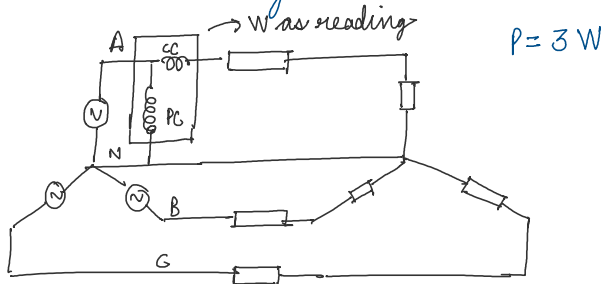

Case 2:- 4-wire unbalanced system


We will need 3 wattmeters to measure power in each phase and then add them all together.

Case 3:- 3 wire - balanced system

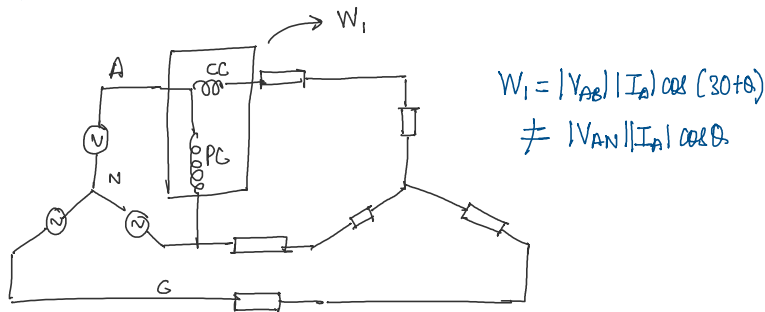


We can't measure using a single wattmeter. We will not be able to connect potential coil to V_{AN} as neutral is not accessible. If we connect as shown in figure above and divide the reading $\sqrt{3}$, then too the θ will be between line voltage & line current & not between phase voltage & line current

* 2 Wattmeter method :-

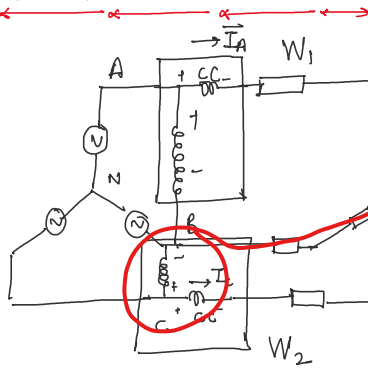

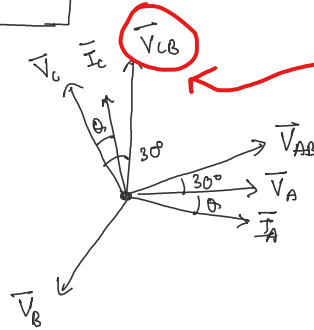Lookout for the polarity of the terminals.
As in case of V_{bc} and V_{cb} .



$$W_1 = |V_{AB}| |I_A| \cos(30 + \theta)$$

$$W_2 = |V_{CB}| |I_C| \cos(30 - \theta)$$


Assuming a balanced system

$$W_1 + W_2 = |V_{AB}| |I_A| [\cos(30 + \theta) + \cos(30 - \theta)]$$

$$= |V_{AB}| |I_A| 2 \cos 30 \cos \theta$$

$$= \sqrt{3} |V_{AB}| |I_A| \cos \theta = P_{3\phi}$$

Case 4: 3 wire unbalanced system

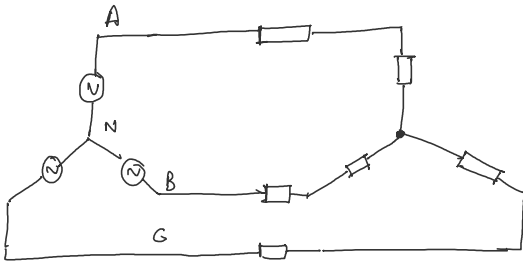

$$W_1 = \frac{1}{T} \int V_{ab} i_a dt$$

$$W_2 = \frac{1}{T} \int V_{cb} i_b dt$$


$$W_1 + W_2 = \frac{1}{T} \int [(V_{an} - V_{bn}) i_a + (V_{cn} - V_{bn}) i_c] dt$$

$$= \frac{1}{T} \int [V_{an} i_a + V_{cn} i_c + V_{bn} i_b + (-V_{bn} i_a - V_{an} i_c - V_{bn} i_b)] dt$$

$$= \frac{1}{T} \int (V_{an} i_a + V_{bn} i_c + V_{cn} i_b) dt = P_{3\phi}$$

Q1. Prove for a balanced 3- ϕ , 3 wire system

$$Q_{3\phi} = \sqrt{3} (W_2 - W_1)$$

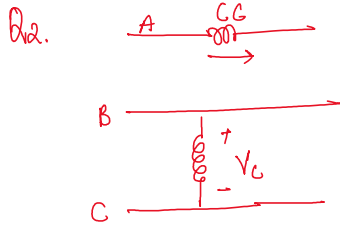

Is the power measured by one wattmeter connected in this manner relate to total real power or reactive power of the balanced system?